

1/2

$$E - Ri(t) - L \frac{di}{dt} = 0$$

$$E = Ri(t) + L \frac{di}{dt}$$

$$\frac{di(t)}{E/R - i(t)} = + \frac{R}{L} \cdot dt$$

$$E - Ri(t) = L \frac{di(t)}{dt}$$

$$\frac{1 dt = \frac{di(t)}{E - Ri(t)}}$$

$$\frac{1 dt = \frac{di(t)}{R \left(\frac{E}{R} - i(t) \right)}}$$

$$\frac{R dt}{L} = \frac{di(t)}{\frac{E}{R} - i(t)}$$

ponieważ

$$z(t) = \frac{E}{R} - i(t)$$

$$dz(t) = -di(t)$$

$$-\frac{dz(t)}{z(t)} = \frac{R}{L} dt$$


$$\frac{dz(t)}{z(t)} = -\frac{R}{L} dt$$

$$\ln z(t) = -\frac{R}{L} \cdot t + \text{const.}$$

$$z(t) = e^{-\frac{R}{L} t} \cdot e^{\text{const.}}$$

$$i(t) = \frac{E}{R} \cdot e^{-\frac{R}{L} t}$$
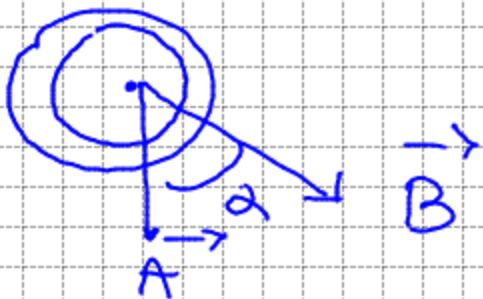
$$i(t) = \frac{E}{R} \left(1 - e^{-\frac{R}{L} t} \right)$$




$$\alpha = \omega t$$

$$\Phi(\vec{B}) = \vec{B} \cdot \vec{A} = B \cdot A \cdot \cos \alpha = B \cdot A \cdot \cos(\omega t)$$

$$\mathcal{E} = - \frac{d\Phi(\vec{B})}{dt} = - \frac{d(B \cdot A \cdot \cos \omega t)}{dt} =$$

$$= \underbrace{B \cdot A \cdot \omega}_{\mathcal{E}_0} \sin \omega t$$

CIRCUITO OHMICO

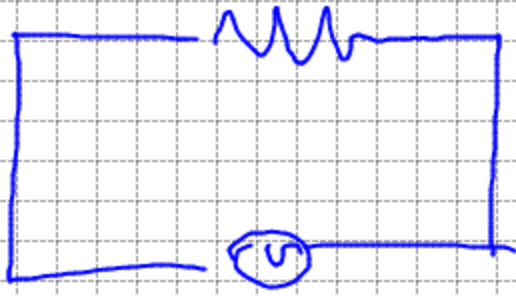


$$R_{eq} = R$$

$$i(t) = \frac{\mathcal{E}}{R} \text{sen } \omega t$$

$$i(t) = i_{max} \text{sen}(2\pi F \cdot t)$$

$$\mathcal{E}(t) = \mathcal{E}_0 \text{sen } \omega t$$

CIRCUITO CAPACITIVO

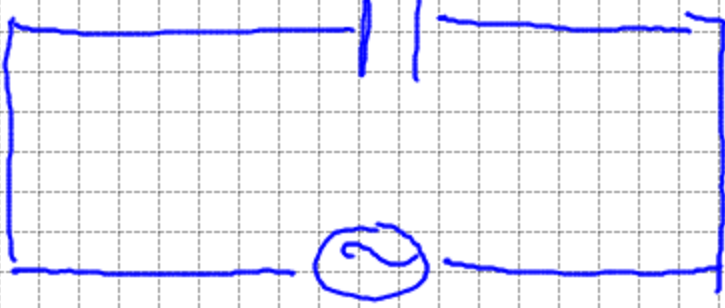

C = capacitat condensator

$$\mathcal{E}_0 \text{sen } \omega t - \frac{Q(t)}{C} = 0$$

$$Q(t) = C \mathcal{E}_0 \text{sen } \omega t$$

$$i(t) = \frac{dQ(t)}{dt}$$

$$i(t) = \frac{d[C \mathcal{E}_0 \text{sen } \omega t]}{dt}$$

$$i(t) = C \mathcal{E}_0 \omega \cos \omega t$$

$$\cos \omega t = \text{sen}\left(\omega t + \frac{\pi}{2}\right)$$

$$i(t) = C \mathcal{E}_0 \omega \cdot \text{sen}\left(\omega t + \frac{\pi}{2}\right)$$


$$i_{max} = C \mathcal{E}_0 \cdot \omega$$

$$i_{max} = \frac{\mathcal{E}_0}{1/\omega C}$$

$$\frac{1}{\omega \cdot C} = X_C$$

$$i_{max} = \frac{\mathcal{E}_0}{X_C}$$

CIRCUITO INDUTIVO

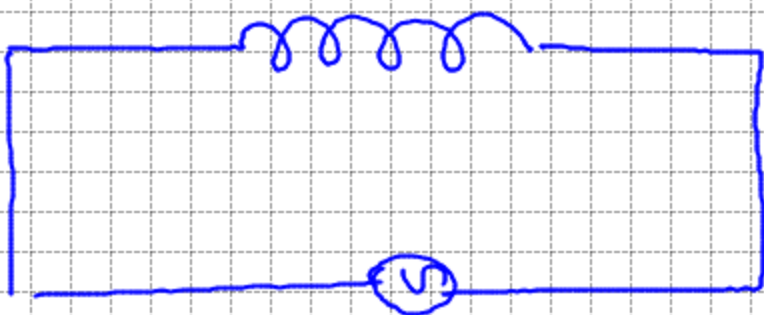

$$-L \frac{di(t)}{dt} + \mathcal{E}_0 \text{sen } \omega t = 0$$